

**Analog Signal Processing (EE60032),**

**Department of Electrical Engineering, Indian Institute of Technology, Kharagpur**

**Tutorial Module 1: Signal Processing Using Operational Amplifier**

**Faculty: Ashis Maity**

**Session: Autumn 2019**

• **Amplifier with different non-idealities**

1. Design an inverting amplifier for a nominal gain of 4, a gain error of 0.1% and an input impedance of 10 k $\Omega$ . [Ans.  $R_2 = 40 \text{ k}\Omega$ ,  $A_{ol} = 5005$ ]

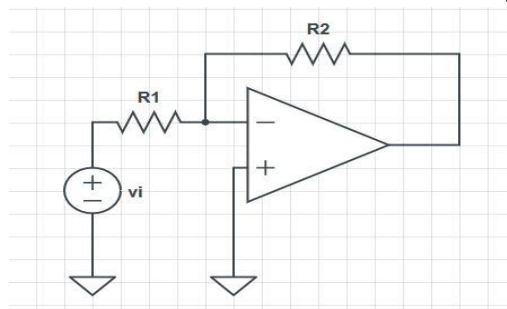


Figure 1

2. Design an inverting amplifier as shown in the figure 2 to get a dc gain of -10 and an input impedance of 10 M $\Omega$ . Calculate  $R_t$ ,  $R_s$  and  $R_1$ . [Ans.  $R_1 = 10 \text{ M}\Omega$ ,  $R_t = 47 \text{ k}\Omega$ ,  $R_s = 22 \Omega$ ]

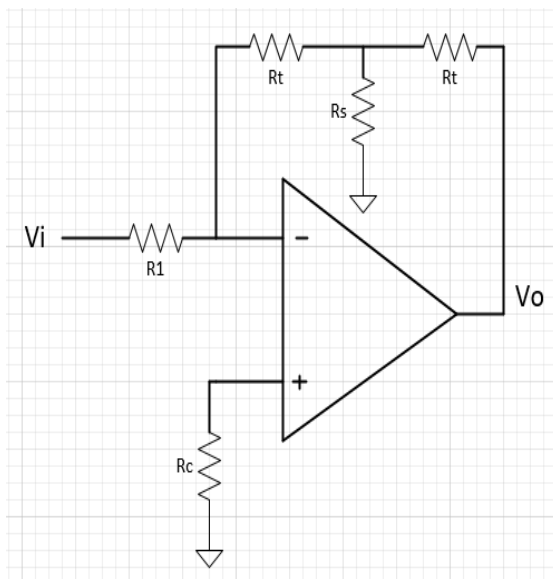


Figure 2

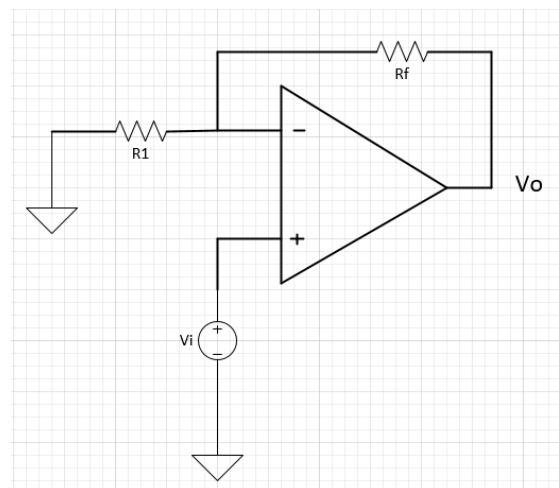


Figure 3

3. For the non-inverting amplifier as shown in the figure 3,  $R_1 = 1 \text{ k}\Omega$ ,  $R_f = 10 \text{ k}\Omega$ .
  - a) Calculate the maximum output offset voltage due to  $V_{ios}$  and  $I_B$ . Assume the op-amp has  $V_{ios} = 10 \text{ mV}$ ,  $I_B = 300 \text{ nA}$  and  $I_{os} = 50 \text{ nA}$ .
  - b) Calculate the value of  $R_{comp}$  needed to reduce the effect of  $I_B$ .
  - c) Calculate the maximum output offset voltage if  $R_{comp}$  as calculated in (b) is connected in the circuit.

[Ans. a) 113 mV, b) 0.9 k $\Omega$ , c) 110.5 mV]

4. In an inverting amplifier  $R_1 = 100 \text{ k}\Omega$ ,  $R_f = 10 \text{ M}\Omega$ . [Ans. a) 606 mV. b) 6 V]
- a) Calculate maximum output offset voltage caused by input offset voltage  $V_{ios}$ ;
- b) Calculate maximum output offset voltage caused by input bias current  $I_B$ ;
- Where  $V_{ios} = 6 \text{ mV}$  and  $I_B = 500 \text{ nA}$ .

• **Adder/Subtractor:**

5. Design a circuit which can generate an output voltage  $v_o = -2(3v_1 + 4v_2 + 2v_3)$ , where  $v_1$ ,  $v_2$  and  $v_3$  are the input voltages.
6. Design an adder circuit using op-amps to get  $v_o = -(0.1v_1 + v_2 + 10v_3)$ , where  $v_1$ ,  $v_2$  and  $v_3$  are the inputs.
7. Find  $V_o$  in figure 4. [Ans. 6.568 V]

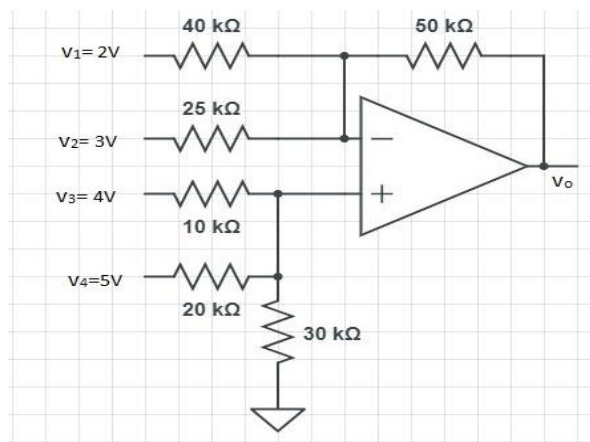


Figure 4

8. Show that  $v_o = a_1v_1 + a_2v_2 + a_3v_3$ . Find  $a_1$ ,  $a_2$  and  $a_3$ . Find the value of  $v_o$  if
- i)  $R_4$  is shorted.
- ii)  $R_4$  is removed.
- iii)  $R_1$  is shorted.

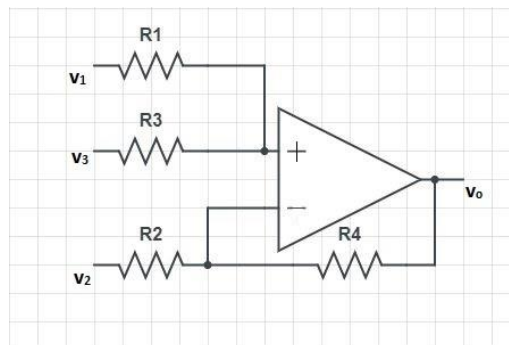


Figure 5

• **Op-amp circuit analysis:**

9. For the instrumentation amplifier shown in the figure 6 below, verify that  $v_o = (1 + R_2/R_1 + 2R_2/R) (v_2 - v_1)$ .

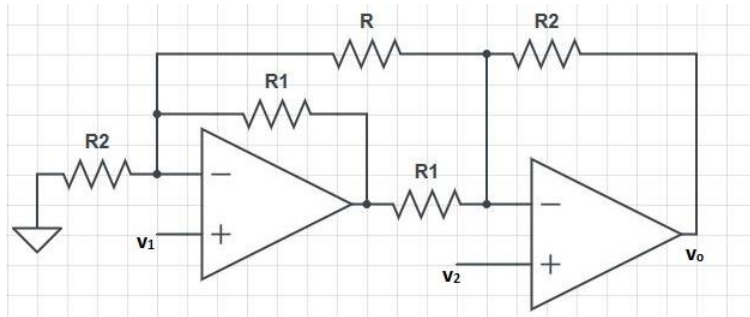


Figure 6

10. Calculate  $V_o$  for the circuit shown in the figure 7 below for  $V_1 = 5V$  and  $V_2 = 2V$ . [Ans. 3V]

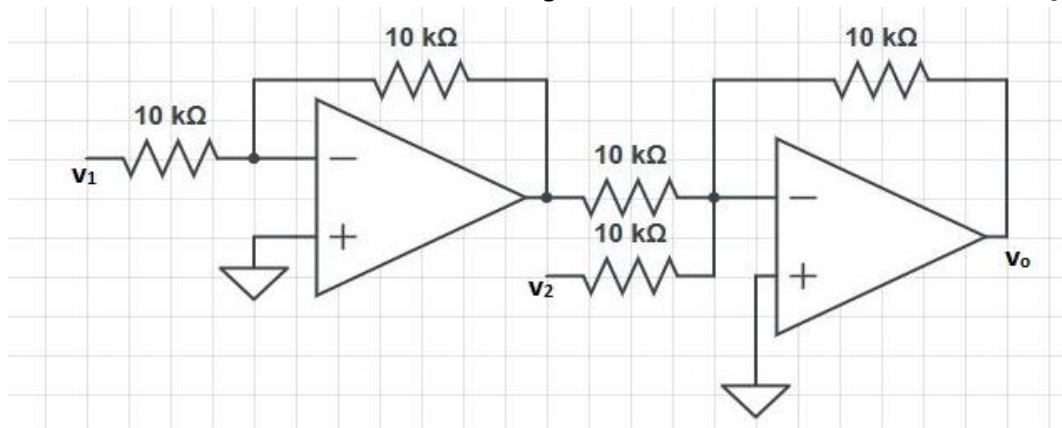


Figure 7

11. Compared with the classical triple op-amp, below in figure 8 uses fewer resistances. The wiper is nominally positioned halfway to maximize the CMRR. Show that  $v_o = (1 + 2R_2/R_1)(v_2 - v_1)$ .

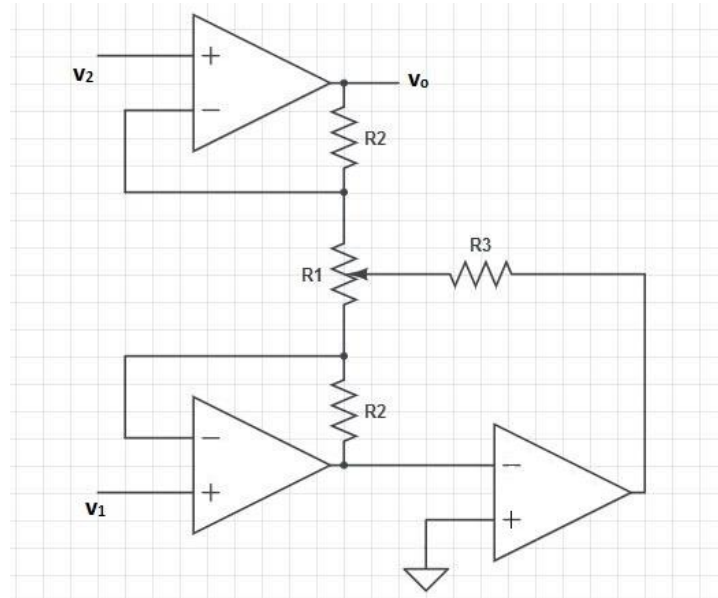


Figure 8

12. Show that  $v_o = 2(1 + R/R_G)(v_2 - v_1)$  in figure 9.

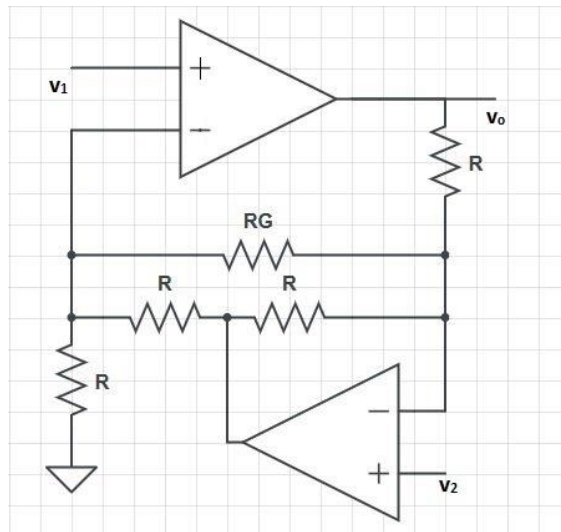


Figure 9

13. The circuit in figure 10 can be used to control the input resistance of the inverting amplifier based on  $OA_1$ .

a) Show that  $R_i = R_1 / (1 - R_1/R_3)$ .

b) Specify resistances suitable for achieving  $A = -10 V/V$  with  $R_i = \infty$ .

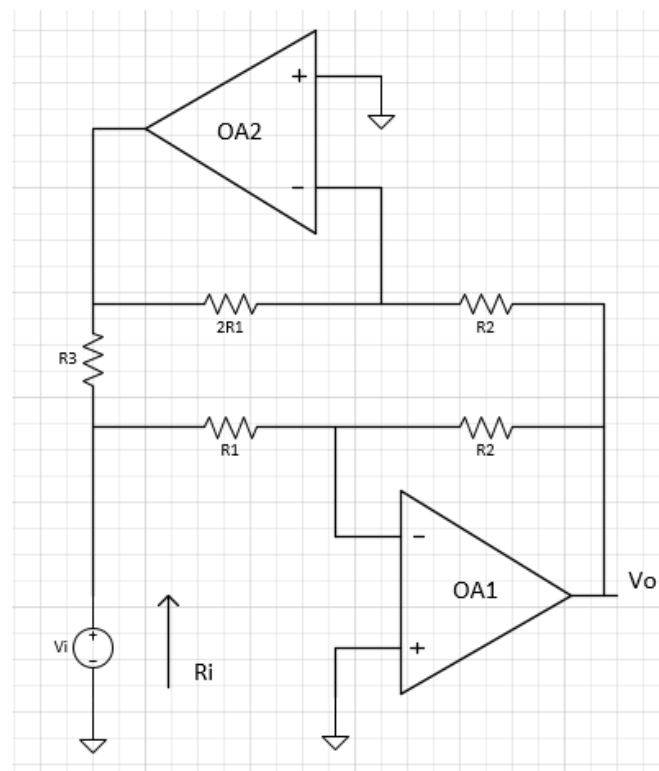


Figure 10

14. In the series-series circuit in figure 11,  $A = 10^4 V/V$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$  and  $R_3 = 3 \text{ k}\Omega$ . Find an expression for  $I_o = A_g V_I - V_L/R_o$ . What is the value of  $A_g$  and  $R_o$ .

[Ans.  $A_g = 2 \times 10^{-3}$ ,  $R_o = 5 \times 10^6$ ]

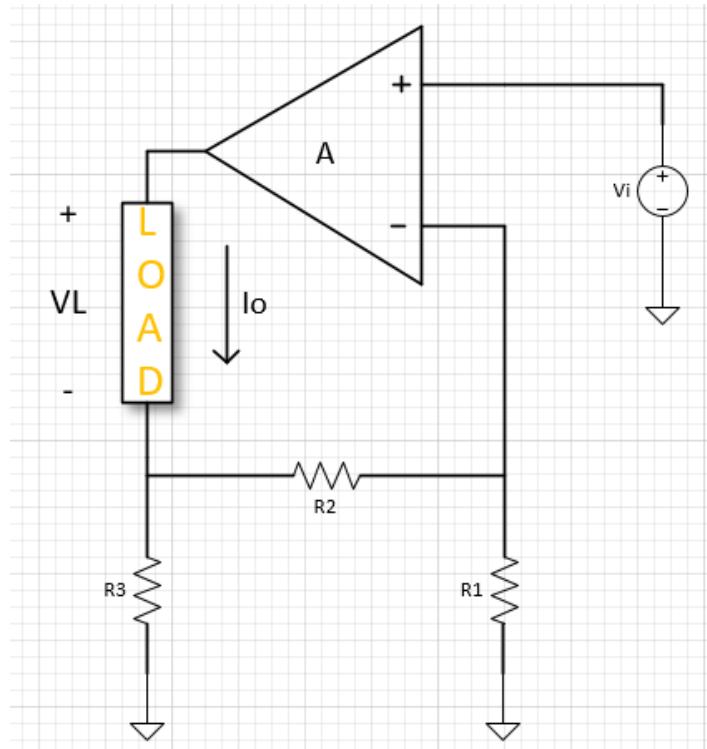


Figure 11

15. Assuming the op-amp of figure 12 has  $r_d = \infty$ ,  $A = 10^3 V/V$  and  $r_o = 0$ , and all resistance are identical.

a) Find  $A_{ideal}$  and gain error GE.

b) Find  $A_{min}$  for  $GE \leq 0.1\%$ . [Ans. a)  $A_{ideal} = -8 V/V$ ,  $GE = 1.28\%$ , b)  $A_{min} = 13000 V/V$ ]

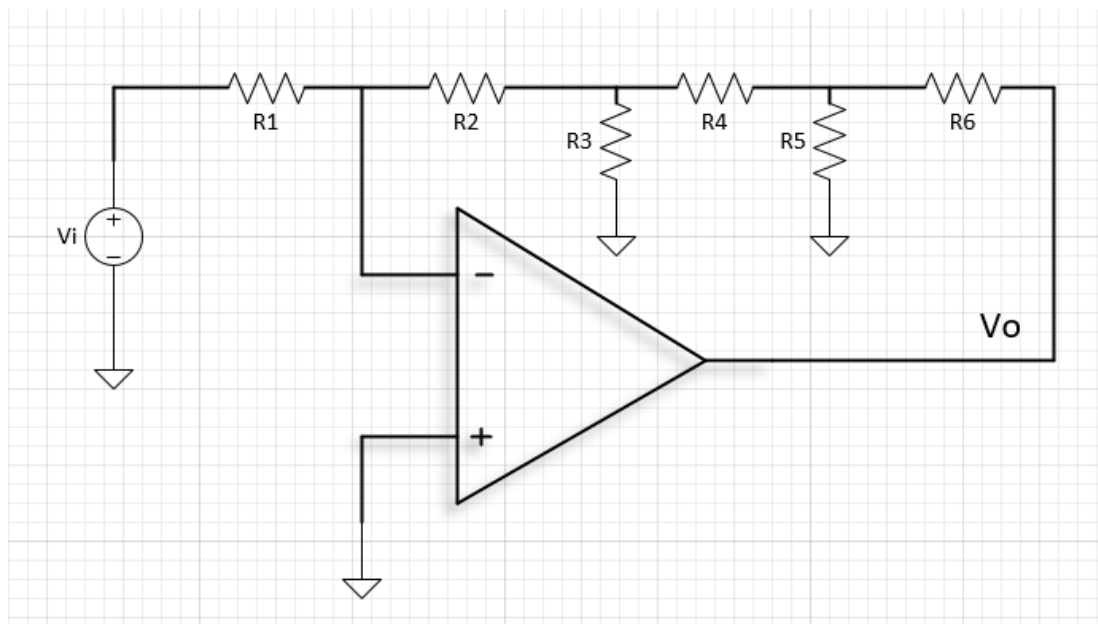


Figure 12

16. The circuit in figure 13 yields  $I_0 = AV_I - (1/R_0)V_L$ . Find the expression for  $A$  and  $R_0$ , as well as the condition among its resistances that yields  $R_0 = \infty$ .

$$[\text{Ans. } A = \frac{(R_1 + R_2)R_4}{R_1 R_5 (R_3 + R_4)}, R_0 = \frac{R_5 R_1 (R_3 + R_4)}{R_1 R_4 - R_2 R_3}, R_0 \rightarrow \infty \text{ for } R_1 R_4 = R_2 R_3]$$

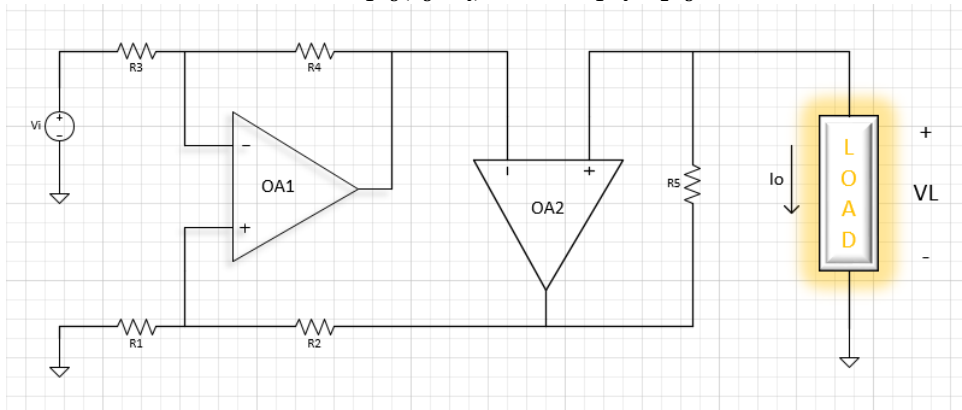


Figure 13

17. Show that the linearized bridge circuit of figure 14 yields  $V_0 = R_2 V_{REF} \delta / R_1$ .

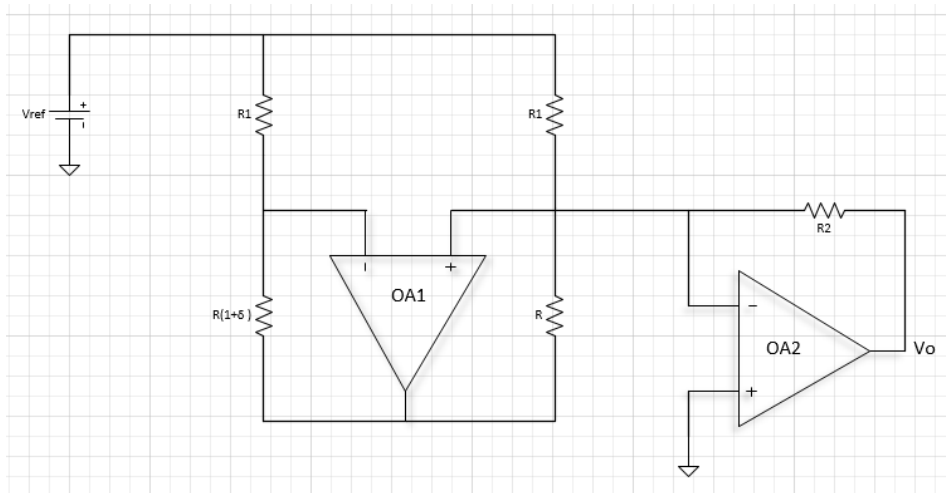


Figure 14

- **Phase-lead/Phase-lag circuit:**

18. Determine the phase angle and the time delay for the circuit shown in the figure 15 for a frequency of 2 kHz. Given:  $R_1 = 20 \text{ k}\Omega$ ,  $R = 39 \text{ k}\Omega$ ,  $R_f = R_1$  and  $C = 1 \text{ nF}$ .

$$[\text{Ans. } \phi = 52.2^\circ, \tau_d = 72.5 \mu\text{s}]$$

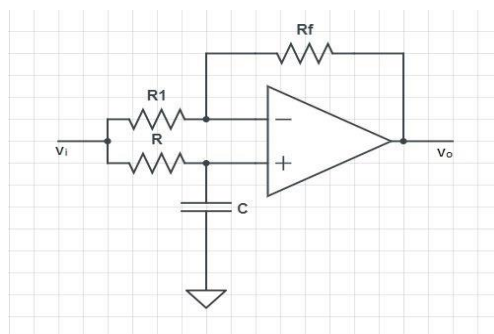


Figure 15

- **Slew rate limitations:**

19. An op-amp used as an inverting amplifier with a gain of 50. The voltage gain vs. frequency curve has a flat gain up to 20 kHz and  $SR=0.5 \text{ V}/\mu\text{S}$ . What maximum peak-to-peak input signal can be applied without distorting the output? [Ans. 3.98 V]
20. A square wave of peak-to-peak amplitude of 500 mV has to be amplified to a peak-to-peak amplitude of 3 V with a rise time of 4  $\mu\text{S}$  or less. Is an op-amp with slew rate of  $0.5 \text{ V}/\mu\text{S}$  sufficient? [Ans.  $SR = 0.6 \text{ V}/\mu\text{s}$ ]
21. a) An op-amp has a slew rate of  $2 \text{ V}/\mu\text{S}$ . What is the maximum frequency of an output sinusoid of peak value 5 V at which distortion sets in due to slew rate limitation?  
b) If a sinusoid of 10 V peak is specified, what is the full power bandwidth?  
[Ans. a) 63.7 k $\Omega$ . b) 31.85 k $\Omega$ ]
22. An op-amp has slew rate of  $2 \text{ V}/\mu\text{S}$ . Find the rise time for an output voltage of 10 V amplitude resulting from a rectangular pulse input if the op-amp is slew rate limited. [Ans. 4  $\mu\text{s}$ ]